 


# Finite Impulse Response Filter VLSI Design

Group: YYYY


Members: Yixiao Du, Yuxiang Long, Yibang Xiao, Yifan Yang

ECE 4740 Course Project



# CONTENTS

 - I. Literature Review
- II. Architecture
- III. Implementation
- IV. Verification and Evaluation




# CONTENTS
 
## I. Literature Review


Adder: CSA, BEC (Binary Excess Converter)

Multiplier: Wallace Tree, CSM (Computation Sharing Memory)




# CONTENTS

## II. Architecture

 

## Figure of Merit

 1. Sampling frequency
2. Precision
3. Power and Area





## Third-order FIR System Diagram

$$X[n] = b_0 * A[n] + b_1 * A[n-1] + b_2 * A[n-2] + b_3 * A[n-3]$$

$$H(z) = b_0 + b_1z^{-1} + b_2z^{-2} + b_3z^{-3}$$


Sample Rate : 100kHz

 


 
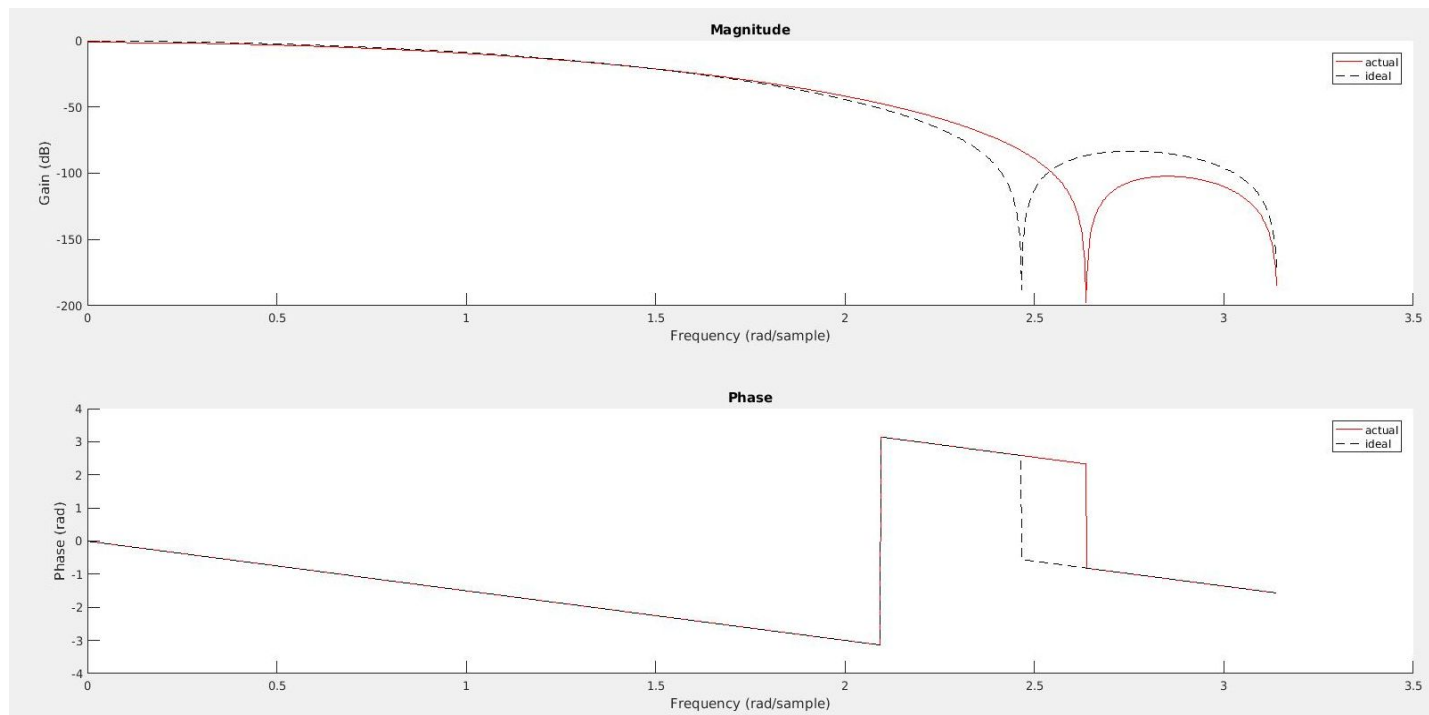
# FIR System Response

b0 =  
0.138336181640625  
b1 =  
0.354217529296875  
b2 =  
0.354217529296875  
b3 =  
0.138336181640625




 


# CONTENTS


## III. Implementation



 


# Top level

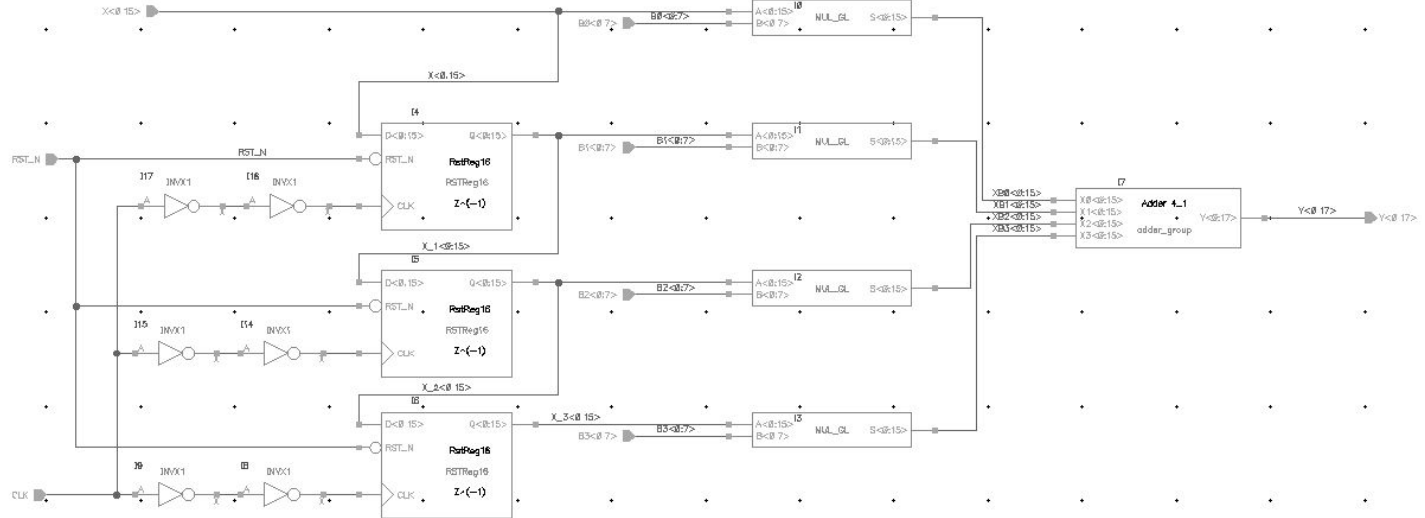


 


## Top level

 


AREA: 206.16\*227.57  $\mu\text{m}^2$

 


**We passed all the DRC and LVS!**

 


# Carry-save 16x8 Multiplier

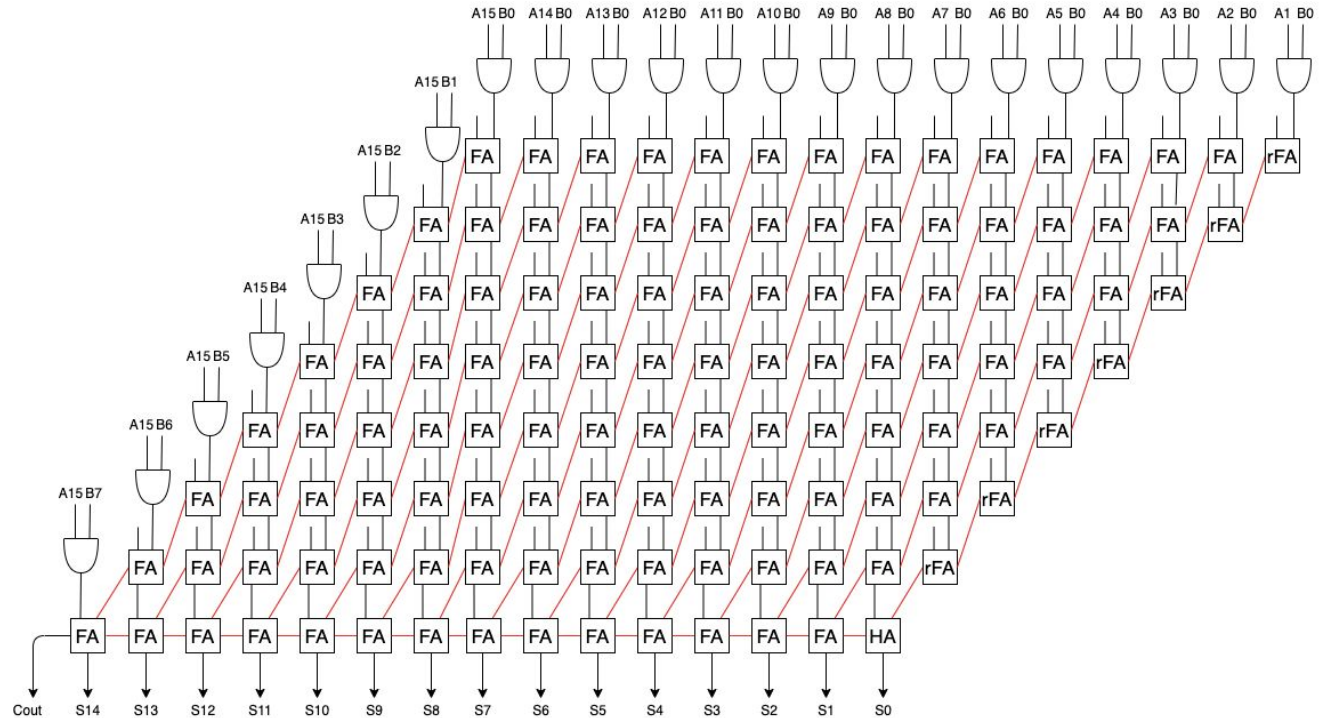

 


# Carry-save 16x8 Multiplier

 


5/20/2020



 


# Carry-save 16x8 Multiplier

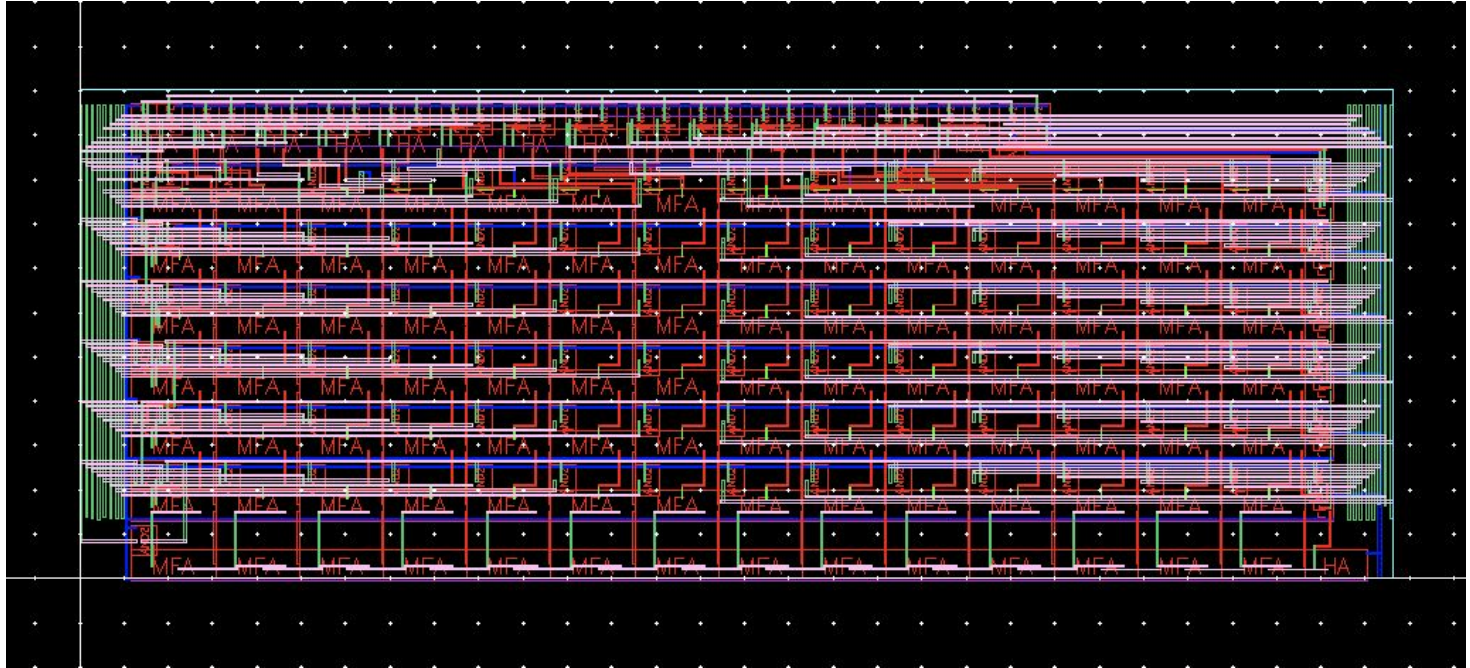


5/20/2020

AREA: 148.19\*55.135  $\mu\text{m}^2$

 


 
# Carry-skip Adder group

16-bit carry-skip adder (from ECE4740 lecture: adder)




adder group

 


 


# Adder group

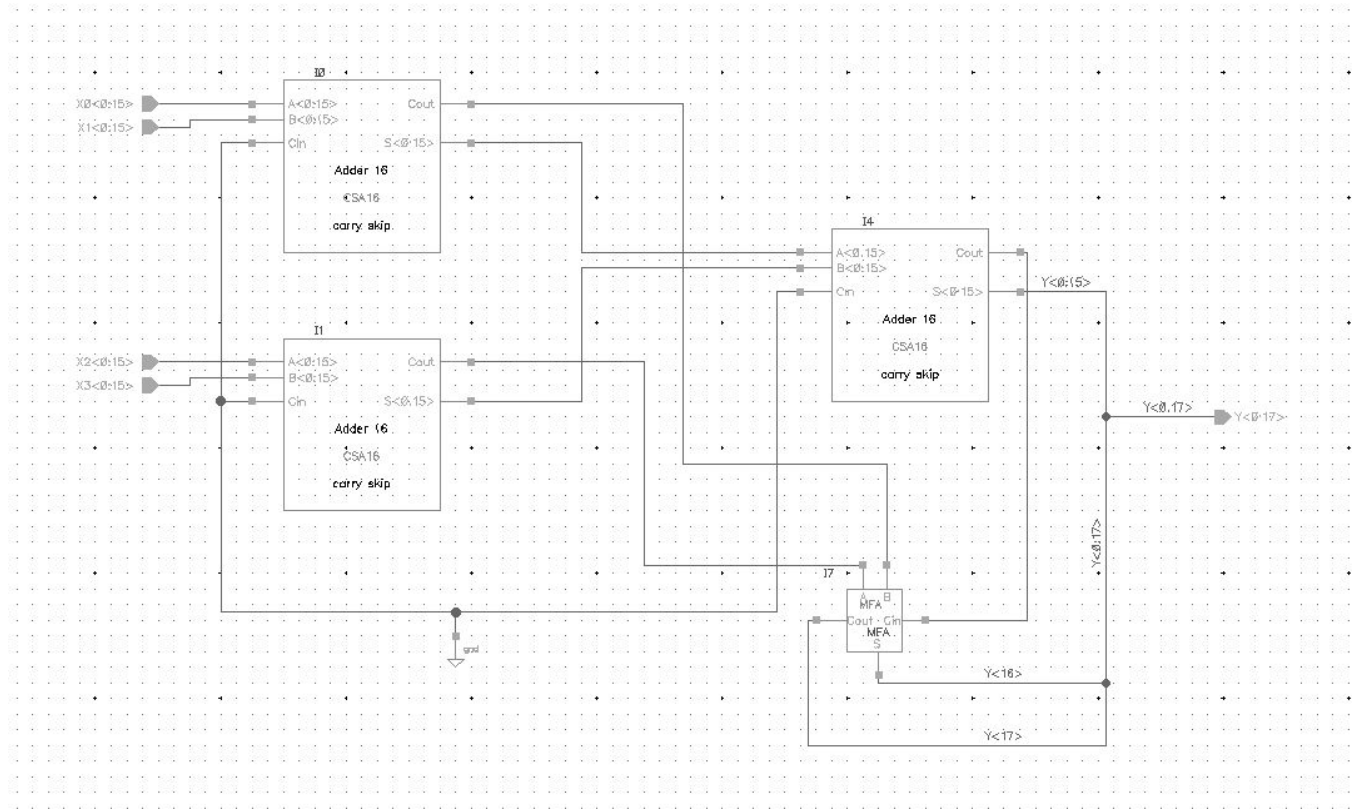



 


## Adder group

 


5/20/2020


AREA: 33.28 \* 72.54um<sup>2</sup>

 


# 16-bit Register with reset


D Flip-flop with reset \* 16

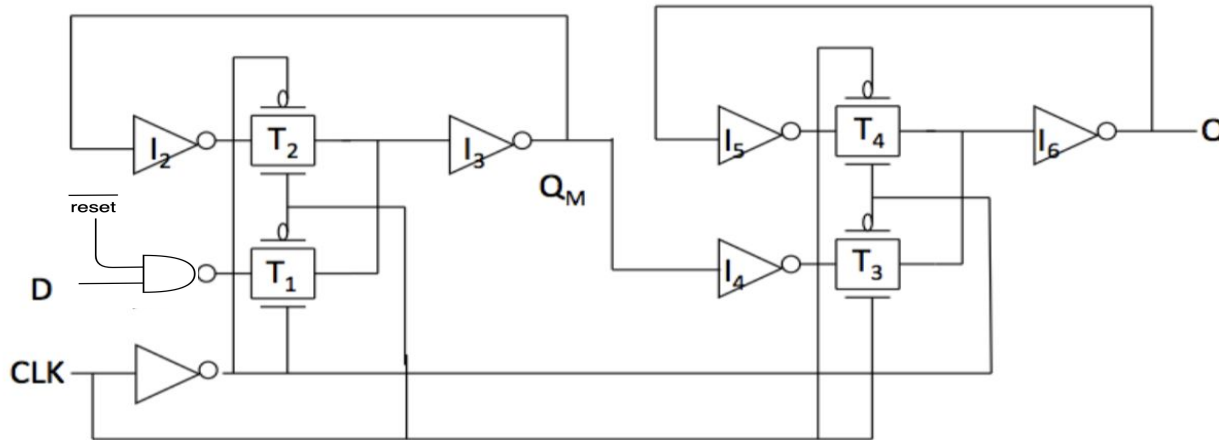

 


# 16-bit Register

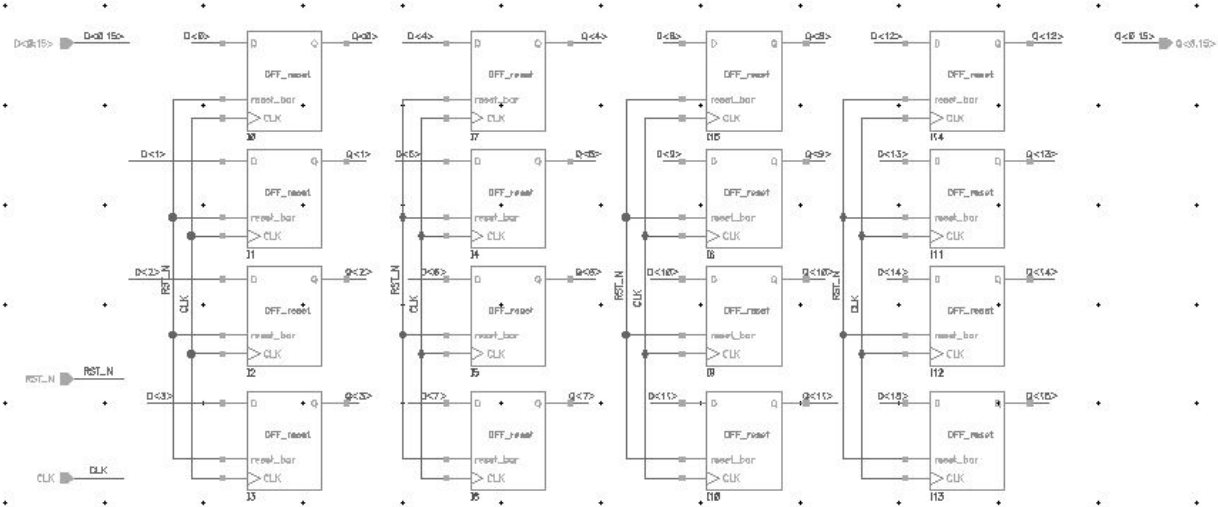

 


# 16-bit Register



 

# CONTENTS

## IV. Verification and Evaluation

 

# Test and Evaluation Strategy

Use Python to auto-generate the VerilogA signal generator

Use VerilogA to apply stimulus to the design under test

Use MATLAB to verify results and post-process data


Unit test : Multiplier, Adder group, Register; directed and random test cases

Static Timing Analysis (not finished)


Unit impulse response, Unit step response, Output to a 10kHz sine wave


AC analysis

Power (not finished)

 


# Testbench - Multiplier

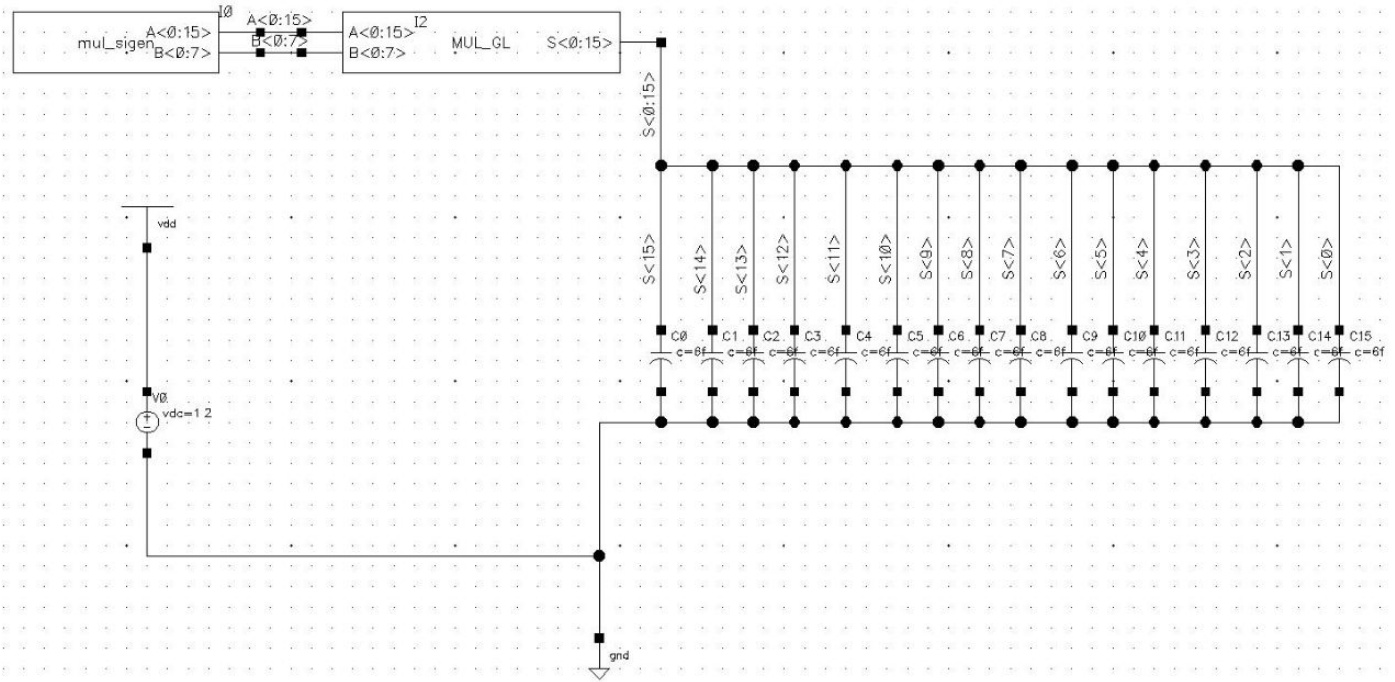


 


# Testbench - Register

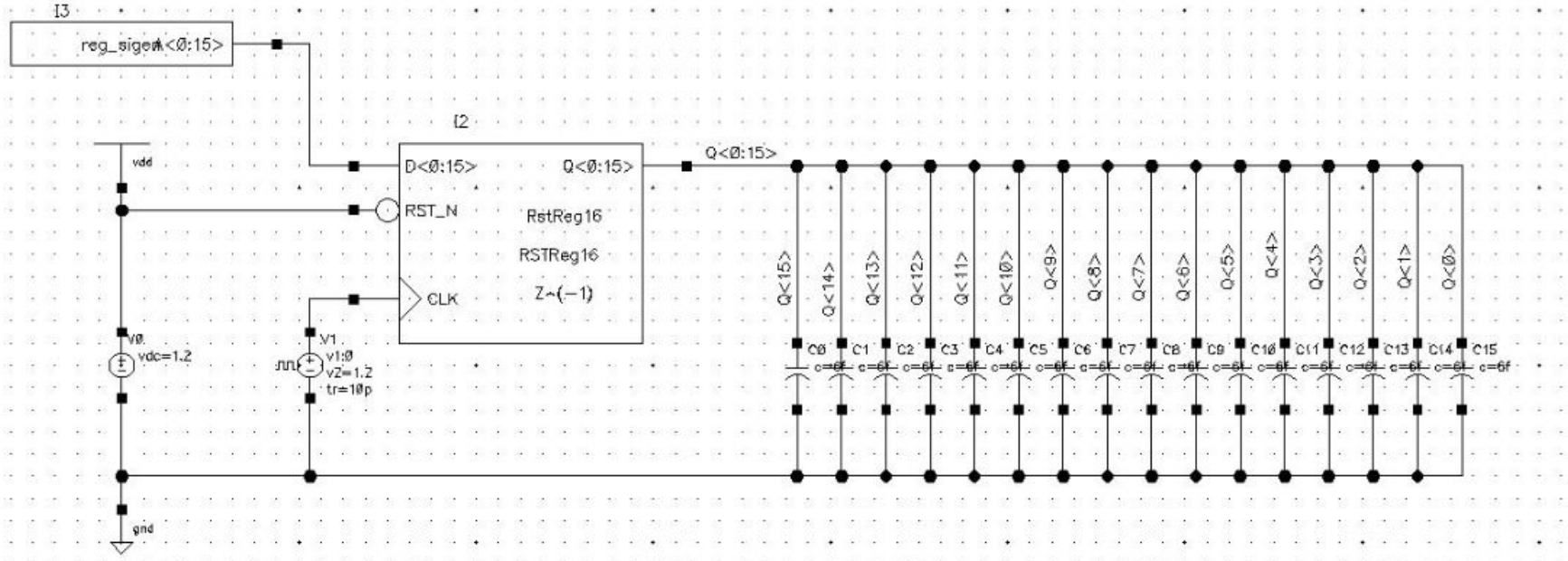




 



# Testbench - Adder Group

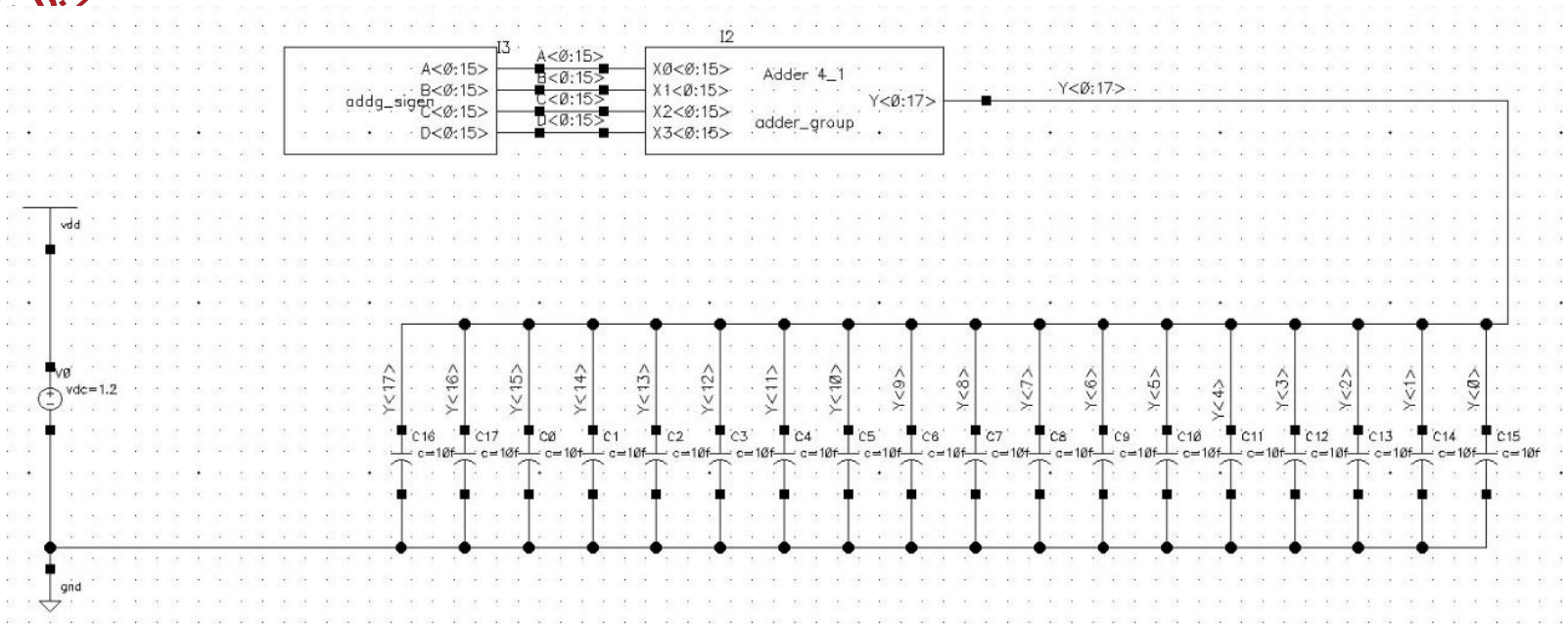

 


# Testbench - FIR Filter

 


 

# Unit tests - Register

 

tpHL	191.37ps
tpLH	200.28ps
tsu	70ps
thd	-40ps

 

# Unit tests - Multiplier

```
caselist = [  
    # name      AAAA      BB  
    [ 'basic0',  0x1234,  0x01],  
    [ 'basic1',  0x7216,  0x12],  
    [ 'basic2',  0xdead,  0x33],  
    [ 'basic3',  0xbeef,  0xff],  
    [ 'basic4',  0xface,  0x00],  
    [ 'basic5',  0xffff,  0xff],  
    [ 'basic6',  0x32de,  0x49],  
    [ 'basic7',  0x1874,  0x99],  
    [ 'basic8',  0x1573,  0xaa],  
    [ 'basic9',  0xdeca,  0xac],  
]  
  
for i in range(10):  
    caselist.append(  
        [ f'random{i}', random.randint(0,0xffff), random.randint(0,0xff)]  
    )
```

```
>> MUL_testing  
A * B = S [S not truncated]
```

```
-----  
1234 * 1 = 12 [1234]
```

```
-----  
7216 * 12 = 805 [8058c]
```

```
-----  
dead * 33 = 2c5c [2c5c77]
```

```
-----  
beef * ff = be30 [be3011]
```

```
-----  
face * 0 = 0 [0]
```

```
-----  
ffff * ff = feff [feff01]
```

```
-----  
32de * 49 = e81 [e814e]
```

```
-----  
1874 * 99 = e9d [e9d54]
```

```
-----  
1573 * aa = e3e [e3e5e]
```

```
-----  
deca * ac = 95af [95afb8]
```

```
-----  
97df * 1c = 109c [109c64]
```

```
-----  
4586 * 53 = 168a [168a72]
```


```
-----  
ff77 * 19 = 18f2 [18f29f]
```

```
-----  
b678 * 6f = 4f1e [4f1e08]
```

```
-----  
d46 * b3 = 947 [947f2]
```

```
-----  
9378 * 13 = af1 [af1e8]
```
 
```
-----  
d276 * b2 = 9256 [92560c]
```



 
# Unit tests - Adder Group

```
caselist = []  
# name      AAAA      BBBB      CCCC      DDDD  
[ 'worst',   0x0001,   0x7fff,   0x8000,   0x0000],  
[ 'basic1',  0x7216,   0x0722,   0x5734,   0x4321],  
[ 'basic2',  0xdead,   0x3ad3,   0xea34,   0x4ff1],  
[ 'basic3',  0xbeef,   0xffff,   0x1234,   0xdd23],  
[ 'basic4',  0xface,   0x0180,   0x1654,   0x4321],  
[ 'basic5',  0xffff,   0x1247,   0x0030,   0x4301],  
[ 'basic6',  0x32de,   0x4915,   0x1034,   0x4321],  
[ 'basic7',  0x1874,   0x4731,   0x4534,   0x0000],  
[ 'basic8',  0x1573,   0xbeee,   0x0034,   0x4321],  
[ 'basic9',  0xdeca,   0xaaaa,   0x0004,   0xdf01],  
]  
  
for i in range(10):  
    caselist.append(  
        [ f'random{i}', random.randint(0,0xffff), random.randint(0,0xffff), random.randint(0,0xffff), random.randint(0,0xffff)]  
    )
```



```
>> ADDG_testing  
Info, results /home/yd383/Cadence/simulation/addg_tb  
A + B + C + D = S  
-----  
1 + 7fff + 8000 + 0 = 10000  
-----  
7216 + 722 + 5734 + 4321 = 1138d  
-----  
dead + 3ad3 + ea34 + 4ff1 = 253a5  
-----  
beef + ffff + 1234 + dd23 = 2ae45  
-----  
face + 180 + 1654 + 4321 = 155c3  
-----  
ffff + 1247 + 30 + 4301 = 15577  
-----  
32de + 4915 + 1034 + 4321 = cf48  
-----  
1874 + 4731 + 4534 + 0 = a4d9  
-----  
1573 + beee + 34 + 4321 = 117b6  
-----  
deca + aaaa + 4 + df01 = 26879  
-----  
5a82 + b524 + 3a3 + 101a = 12363  
-----  
ebf6 + aef8 + 869d + 35e9 = 25774  
-----  
6822 + 7a02 + 9418 + a8b = 180c7  
-----  
6a3b + a2f5 + 254b + b095 = 1e310  
-----  
3ab0 + b970 + 4d1c + e933 = 22a6f  
-----  
b408 + 891a + d8cd + 58b7 = 26ea6  
-----
```






  
# Unit tests - Adder Group - Worst Case


```
>> ADDG_testing
Info, results /home/yd383/Cadence/simulation/addg_tb
A + B + C + D = S
-----
1 + 7fff + 8000 + 0 = 10000
-----
```



 


# Unit Impulse Response

 


 


# Unit Step Response

 




 



## Sine Wave Input - Output

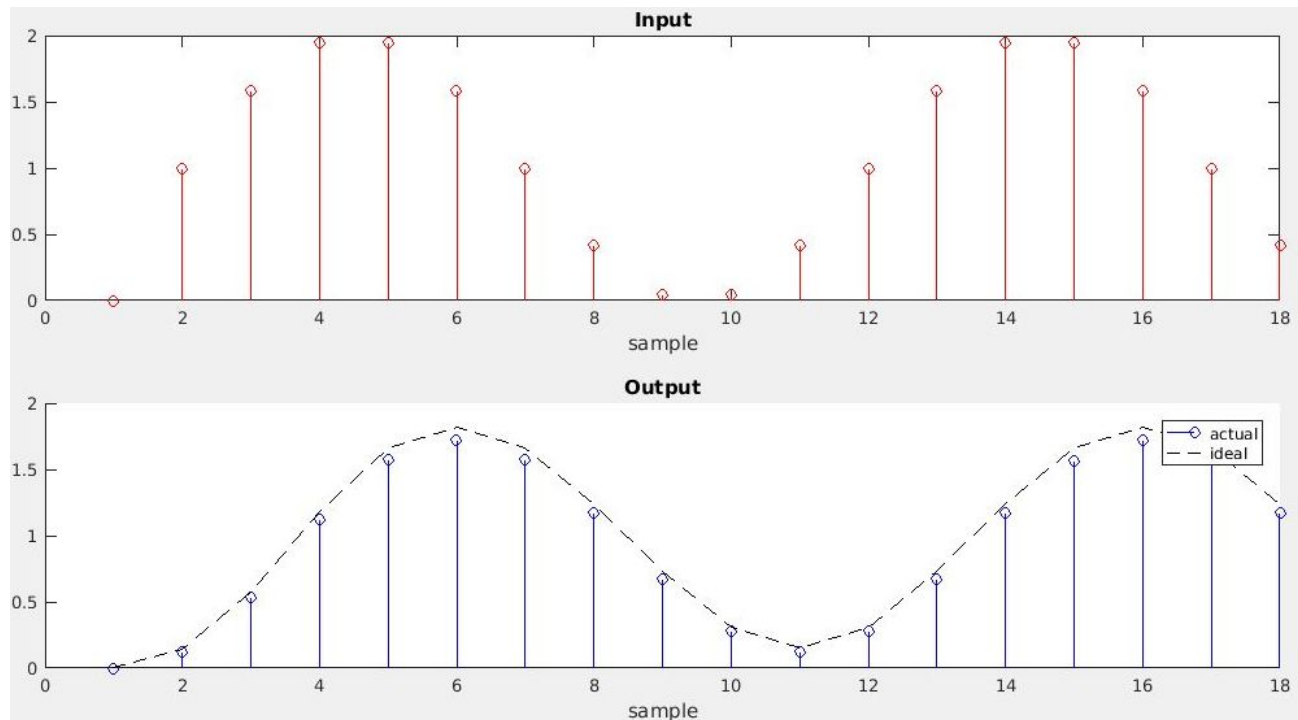

 

# Frequency Response

 

 

## Members' contribution

Yixiao Du (yd383)	Architecture, Adder group, Register, Test and verification
Yibang Xiao (yx455)	Multiplier Architecture and layout design, reduced HA, final FIR layout
Yuxiang Long (yl3377)	Multiplier design, reduced FA, FIR layout
Yifan Yang (yy887)	D Flip-flop, Buffer tree, participated in Multiplier layout design